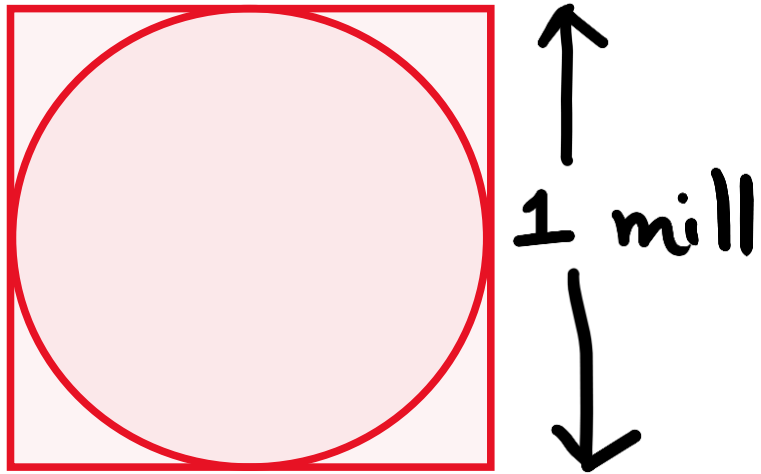


# **ELECTRICAL CIRCUITS**


Jubair Ahammad Akter

Undergraduate Student of B.Sc.(CSE)


University of Dhaka



$$1000 \text{ mill} = 1 \text{ inch}$$

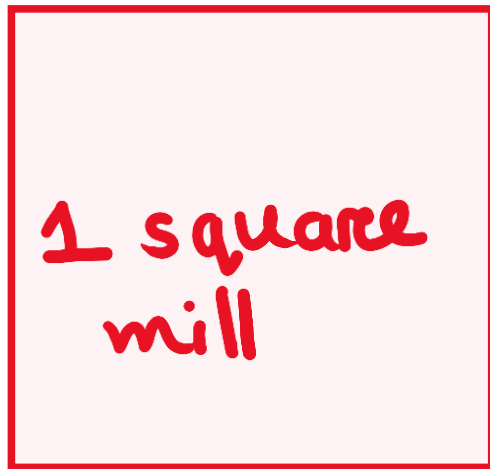


1 SM

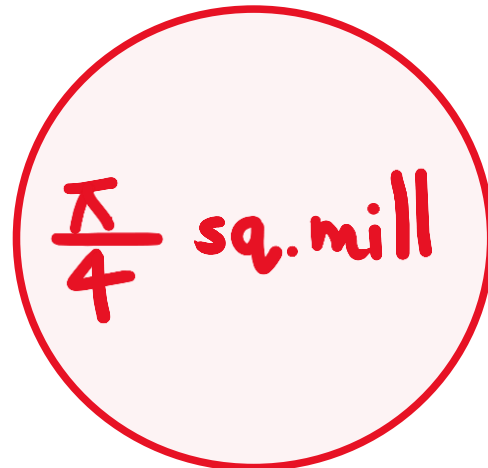

1 CM

$$\therefore 1 \text{ CM} = \frac{\pi}{4} \text{ SM}$$

Square Mill vs Circular Mill

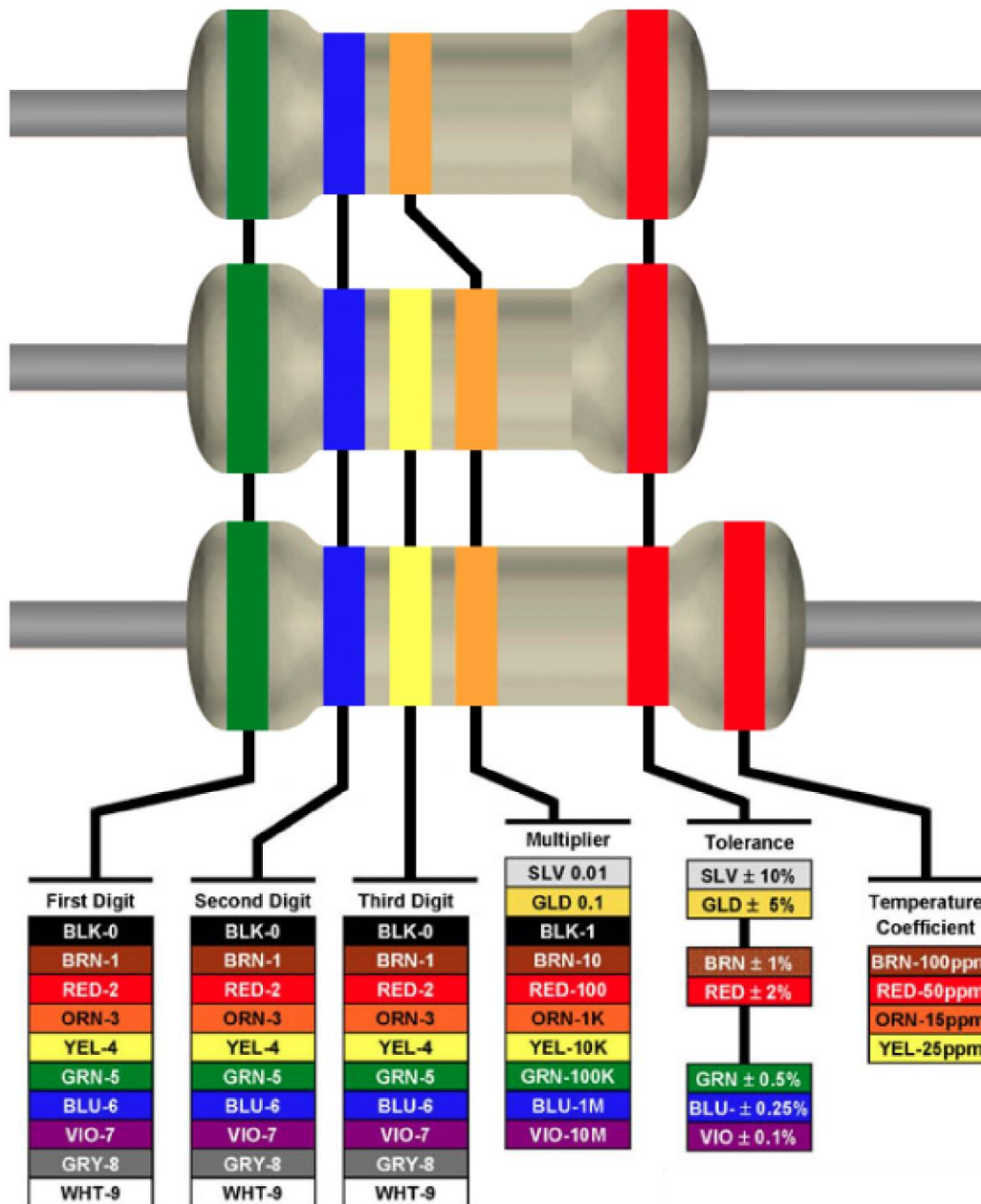

$$56000 \times 2\% = 1120$$

$$56000 - 1120 = 54880$$

$$56000 + 1120 = 57120$$

$$54880 - 57120 \text{ (Ans)}$$

$$564000 \times 2\% = 11280$$

$$564000 - 11280 = 552720$$

$$564000 + 11280 = 575280$$

$$552720 - 575280 \text{ (Ans)}$$

$$564000 \times 2\% = 11280$$

$$564000 - 11280 = 552720$$

$$564000 + 11280 = 575280$$

$$552720 - 575280 \text{ (Ans)}$$

**Color code of a resistance**

$$R = \rho \frac{L}{A}$$

$$V = IR$$


$$W = QV$$

$$Q = It$$

$$P = \frac{W}{t} = \frac{QV}{t} = VI = \frac{V^2}{R} = I^2 R$$


$$1 \text{ watt} = 1 \text{ J/s}$$

$$1 \text{ HP} = 746 \text{ watts}$$

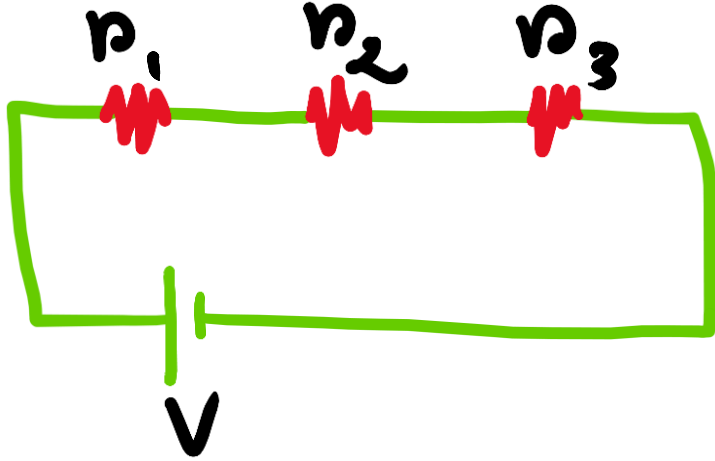

$$r_s = r_1 + r_2 + r_3$$

$$P_s = P_1 + P_2 + P_3$$

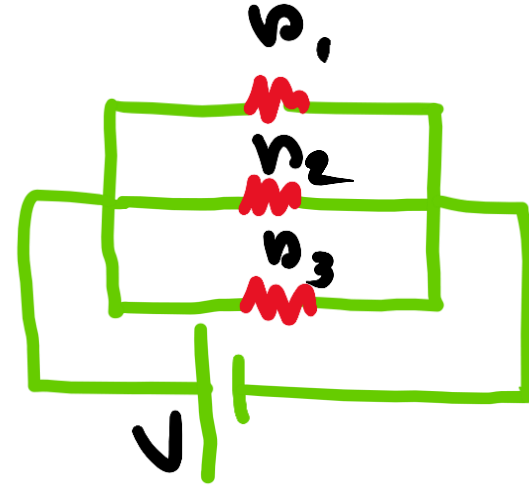


$$\frac{1}{r_p} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}$$


$$\frac{1}{P_v} = \frac{1}{P_1} + \frac{1}{P_2} + \frac{1}{P_3}$$

# Difference between voltage and voltage difference

$$V_A - V_B = IR$$

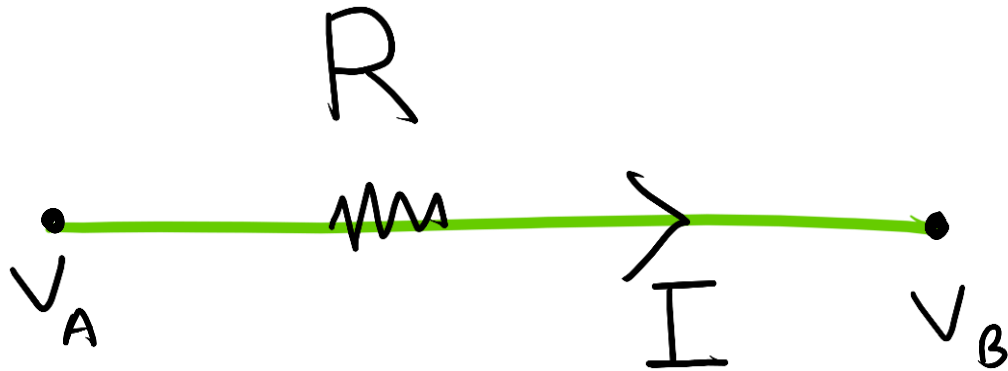
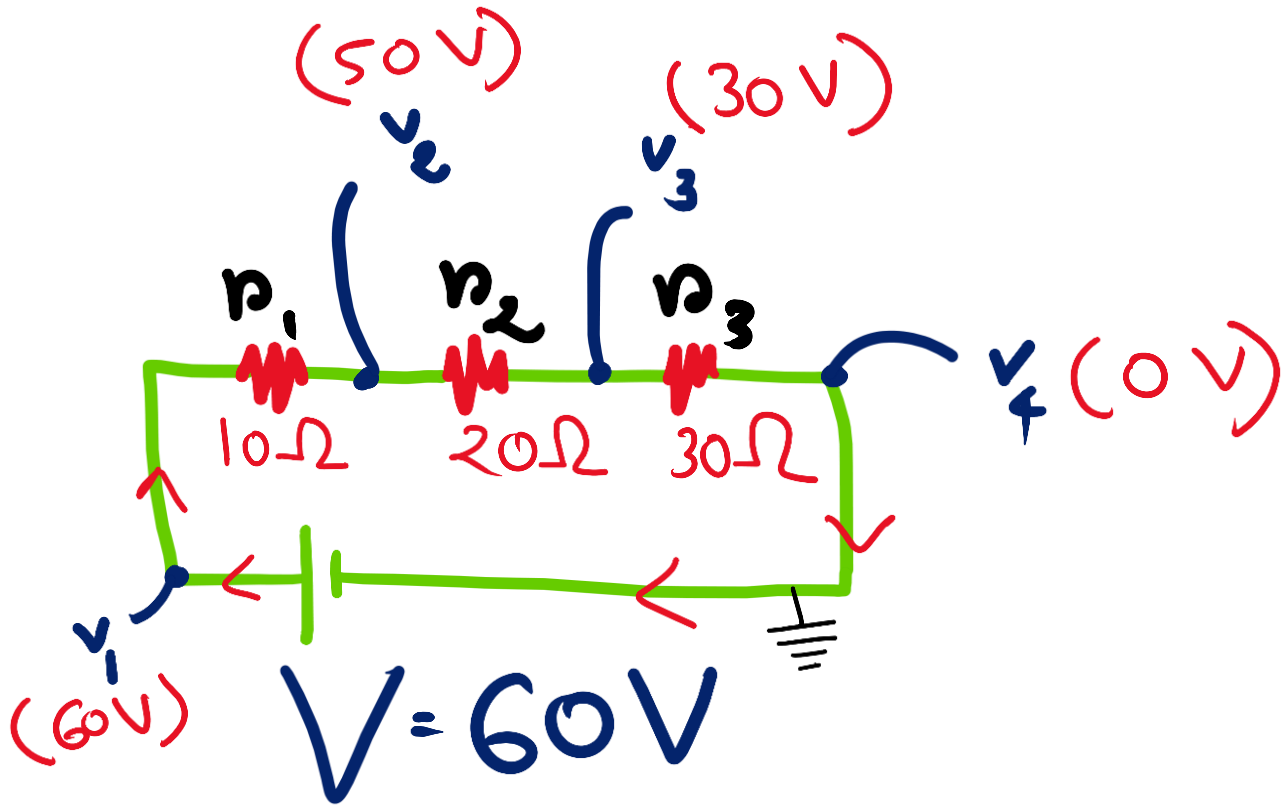
# Difference between voltage and voltage difference



$$V_1 - V_2 = I r_1$$


$$V_2 - V_3 = I r_2$$

$$V_3 - V_4 = I r_3$$

$$V_1 - V_4 = 60$$

$V_1 =$	60V	$v_2 =$	50V	$v_3 =$	30V	$v_4 =$	0V
---------	-----	---------	-----	---------	-----	---------	----
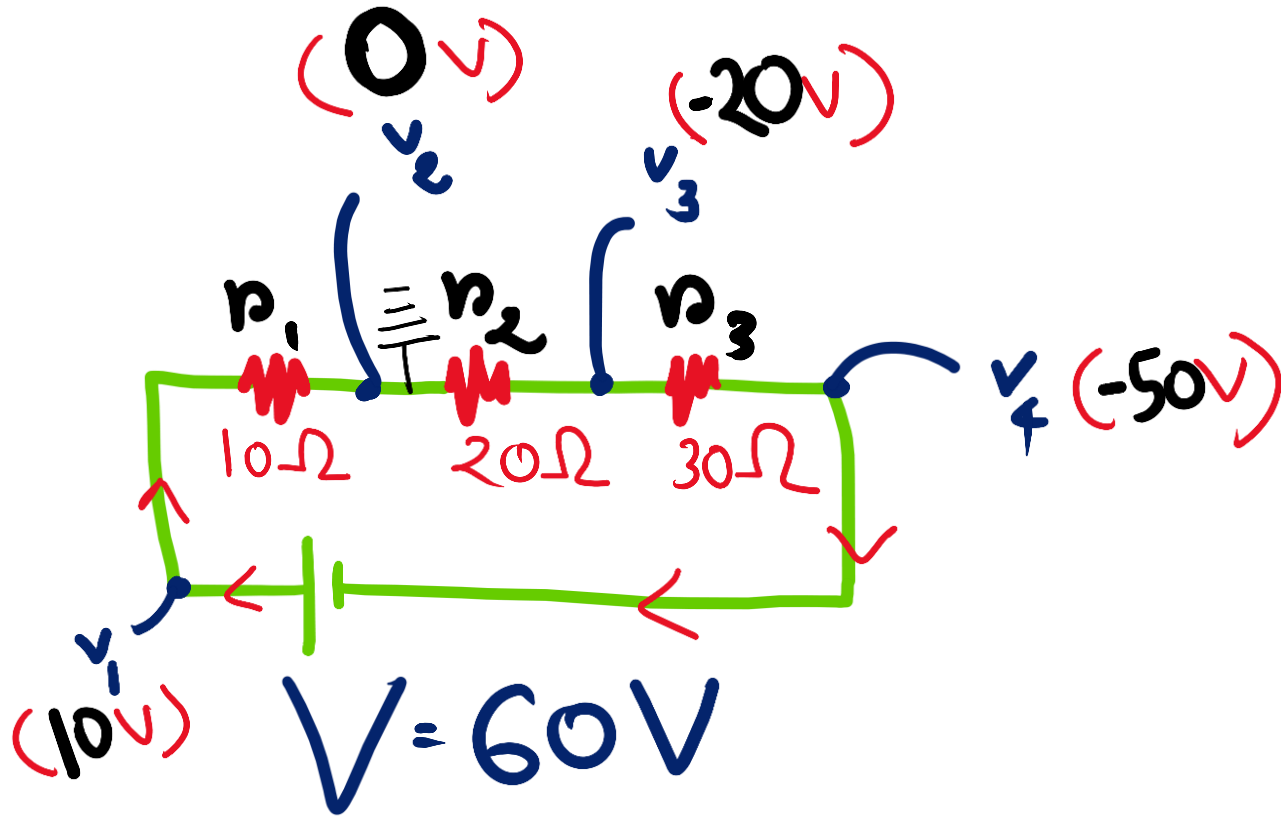
# Difference between voltage and voltage difference



$$V_1 - V_2 = I R_1$$

$$V_2 - V_3 = I R_2$$


$$V_3 - V_4 = I R_3$$

$$V_1 - V_4 = 60$$

$V_1 =$	10V	$v_2 =$	0V	$v_3 =$	-20V	$v_4 =$	-50V
---------	-----	---------	----	---------	------	---------	------




## Voltage divider Rule

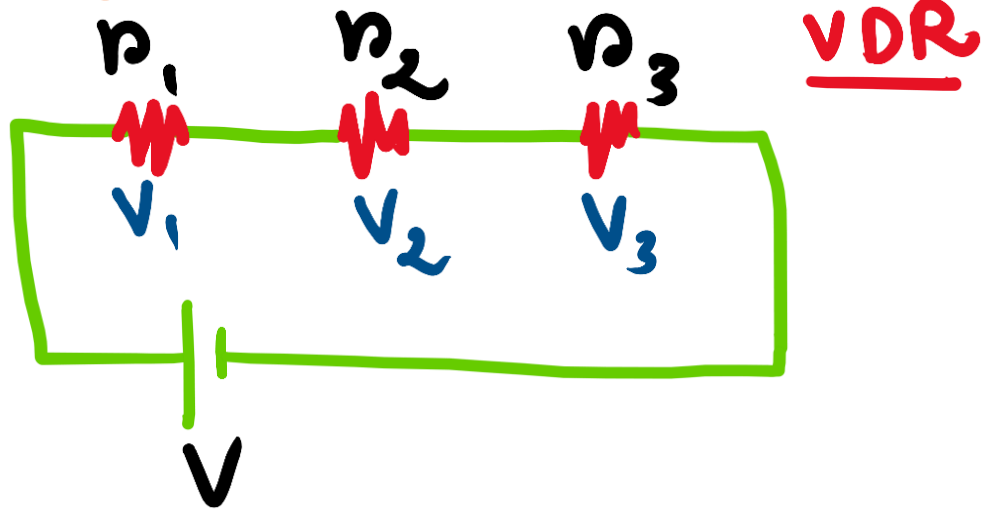

$$\frac{V}{r_T} = \frac{V_1}{r_1} = \frac{V_2}{r_2} = \frac{V_3}{r_3}$$

$$\therefore V_x = \frac{r_x}{r_T} \cdot V$$


## Current Divider Rule

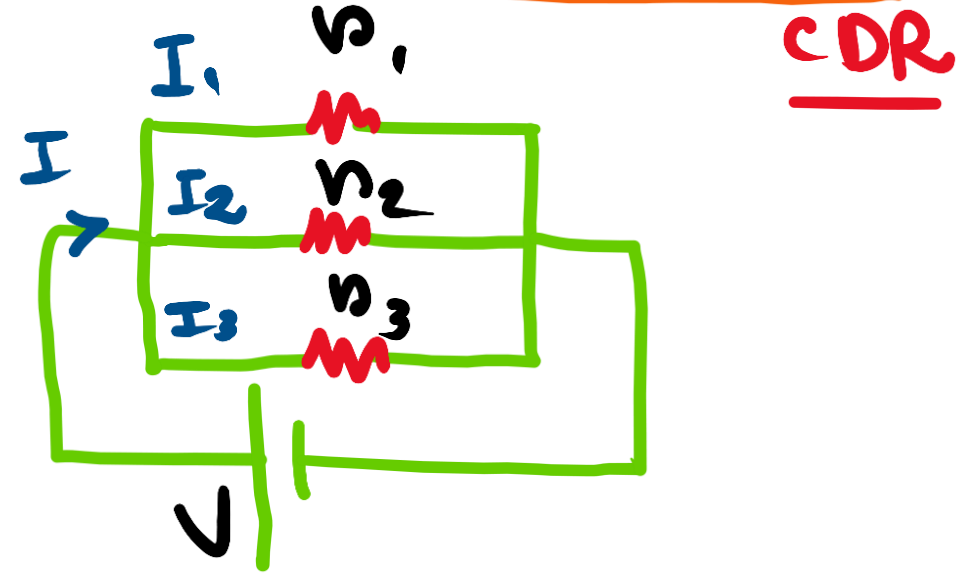

$$V = I r_P = I_1 r_1 = I_2 r_2 = I_3 r_3 \dots$$

$$I_x = \frac{r_P}{r_x} \cdot I$$

# CDR with two Resistance only

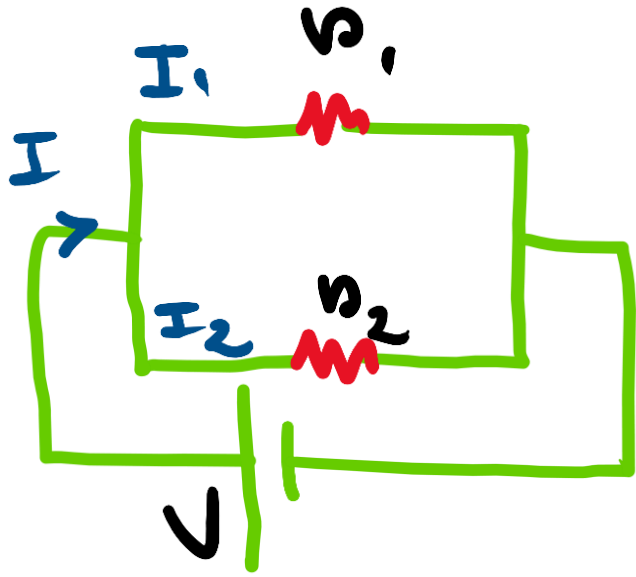


$$V = I r_p = I_1 r_1 = I_2 r_2$$

$$= I \frac{r_1 r_2}{r_1 + r_2} = I_1 r_1 = I_2 r_2$$


$$\therefore I_1 = I \frac{r_2}{r_1 + r_2}$$

$$\therefore I_2 = I \frac{r_1}{r_1 + r_2}$$

# Source Conversion

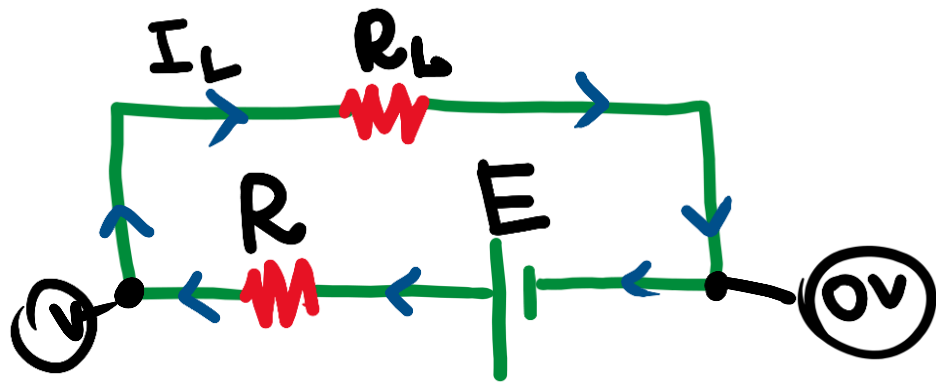

$$E - I_L R = V \quad \text{--- (i)}$$

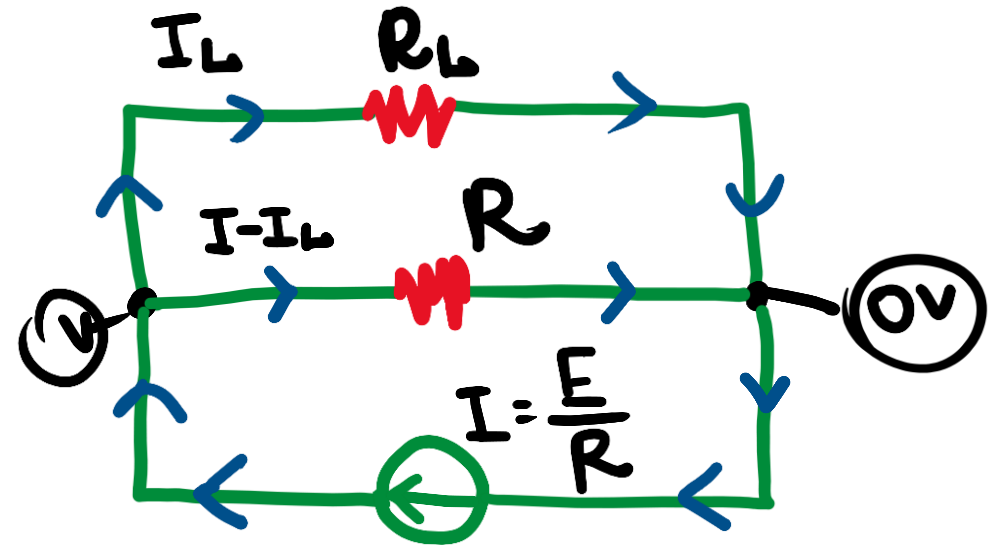


$$V = I_L R_L = (I - I_L) R$$
$$\therefore V = IR - I_L R \quad \text{--- (ii)}$$

from (i) & (ii),  $E - I_L R = IR - I_L R$   
 $\therefore E = IR$

$$\therefore I = \frac{E}{R}$$

$\Delta \longleftrightarrow Y$  transform

---

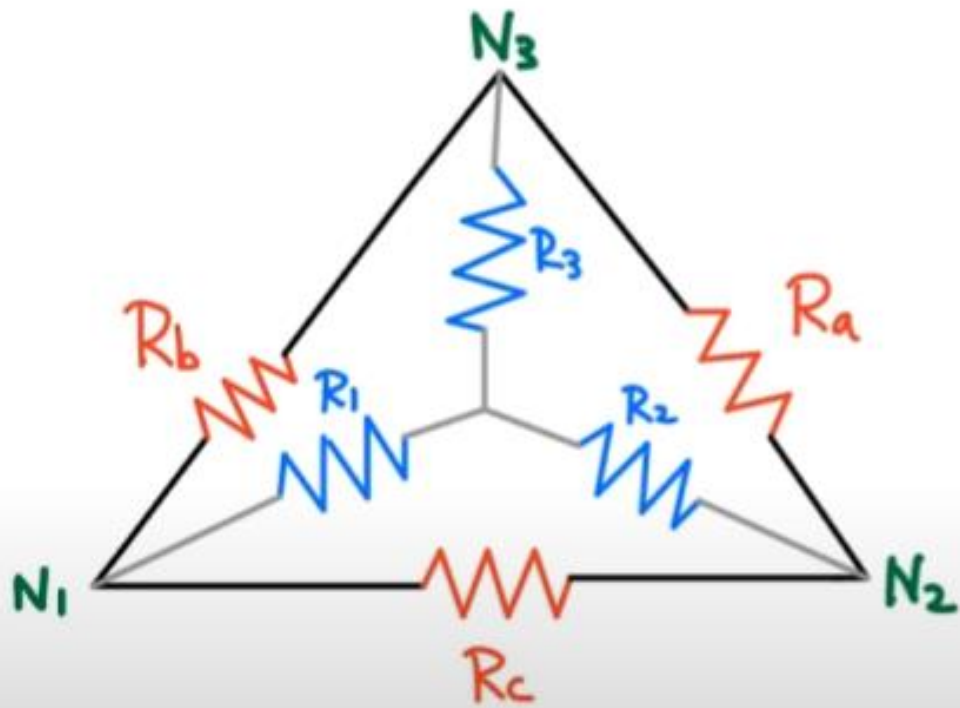

$Y \leftarrow \Delta$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$



$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$\Delta \leftarrow Y$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
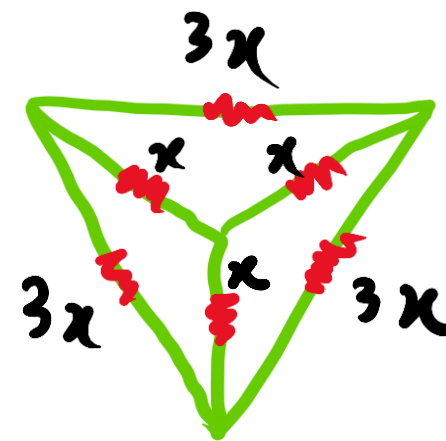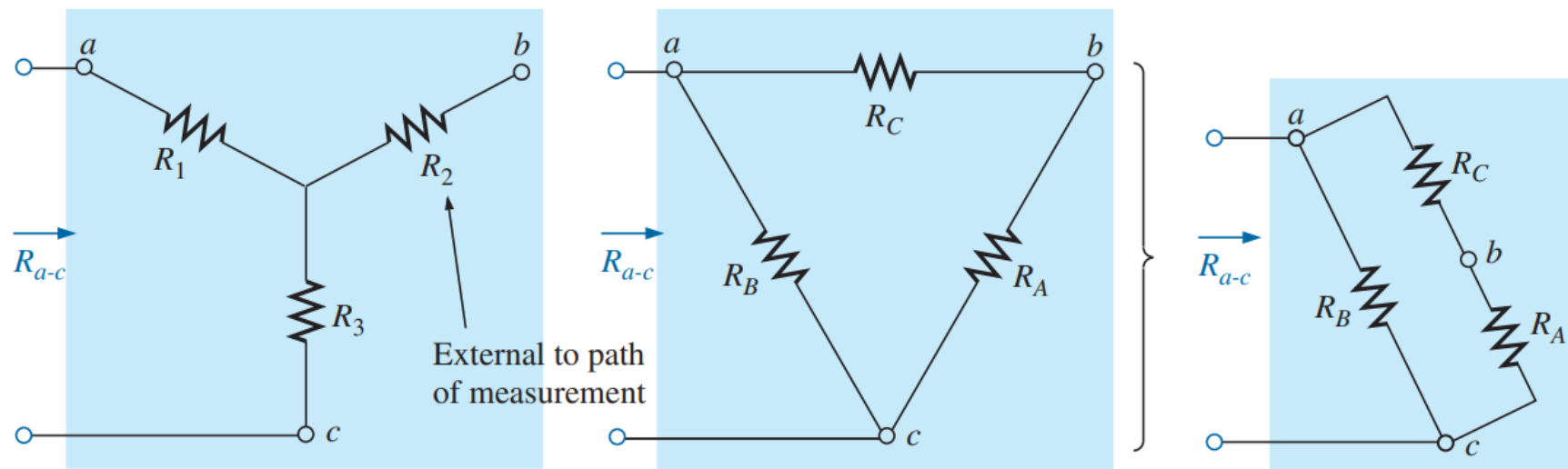
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



$$R_{a-c} = R_1 + R_3 = \frac{R_B(R_A + R_C)}{R_B + (R_A + R_C)}$$


$$R_{a-b} = R_1 + R_2 = \frac{R_C(R_A + R_B)}{R_C + (R_A + R_B)}$$

$$R_{b-c} = R_2 + R_3 = \frac{R_A(R_B + R_C)}{R_A + (R_B + R_C)}$$

$$\begin{aligned} Y &\leftarrow \Delta \\ R_1 &= \frac{R_b R_c}{R_a + R_b + R_c} \\ R_2 &= \frac{R_a R_c}{R_a + R_b + R_c} \\ R_3 &= \frac{R_a R_b}{R_a + R_b + R_c} \end{aligned}$$

$$\begin{aligned} \Delta &\leftarrow Y \\ R_a &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \\ R_b &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_c &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \end{aligned}$$

# Mesh Analysis

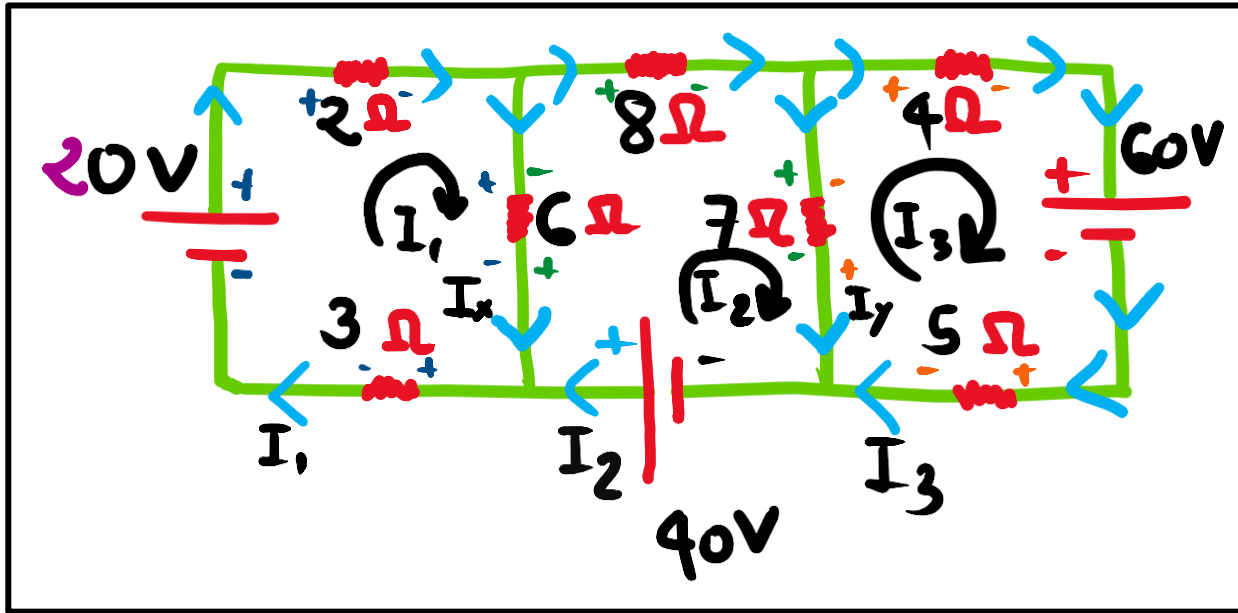

$$I_x = I_1 - I_2$$

$$I_y = I_2 - I_3$$


## [Format Approach]

$$\begin{aligned} (2+3+6)I_1 + (-6)I_2 + 0 \cdot I_3 - 20 &= 0 \\ (-6)I_1 + (6+8+7)I_2 + (-7)I_3 - 40 &= 0 \\ 0 \cdot I_1 + (-7)I_2 + (5+7+4)I_3 + 60 &= 0 \end{aligned}$$

## [Normal Approach]

$$\begin{aligned} 2I_1 + 6(I_1 - I_2) + 3I_1 - 20 &= 0 \\ 6(I_2 - I_1) + 8I_2 + 7(I_2 - I_3) - 40 &= 0 \\ 7(I_3 - I_2) + 5I_3 + 4I_3 + 60 &= 0 \end{aligned}$$


# Super Mesh

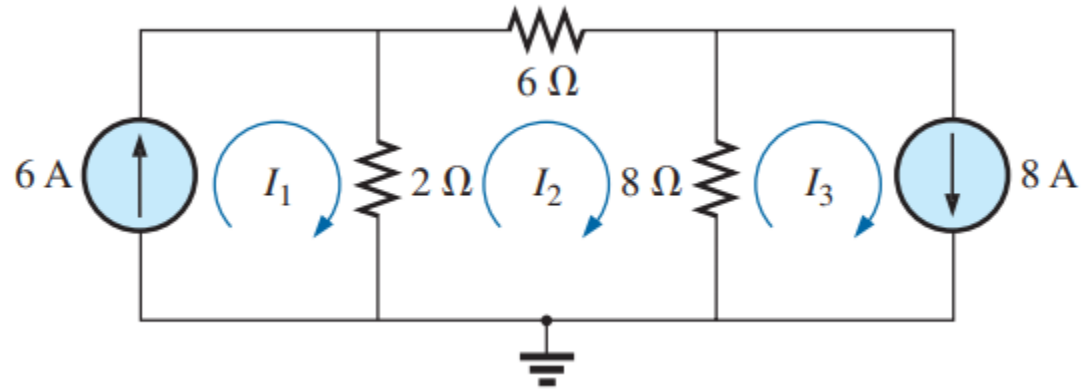

**Solution:** The mesh currents are defined in Fig. 8.37. The current sources are removed, and the single supermesh path is defined in Fig. 8.38.

Applying Kirchhoff's voltage law around the supermesh path:
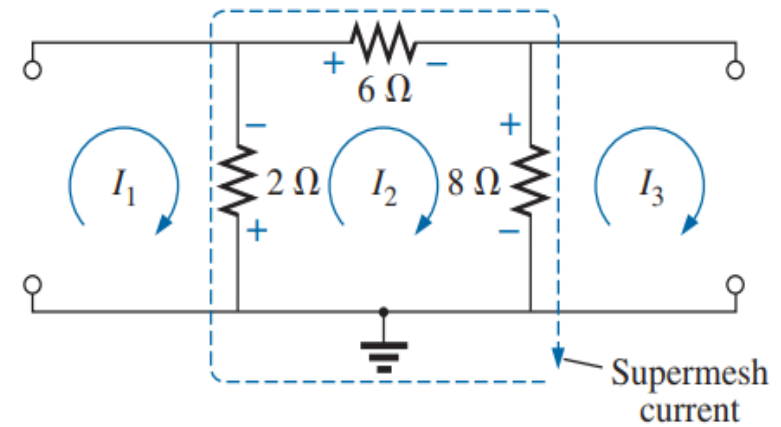
$$\begin{aligned} -V_{2\Omega} - V_{6\Omega} - V_{8\Omega} &= 0 \\ -(I_2 - I_1)2\Omega - I_2(6\Omega) - (I_2 - I_3)8\Omega &= 0 \\ -2I_2 + 2I_1 - 6I_2 - 8I_2 + 8I_3 &= 0 \\ 2I_1 - 16I_2 + 8I_3 &= 0 \end{aligned}$$



Introducing the relationship between the mesh currents and the current sources:

$$\begin{aligned} I_1 &= 6\text{ A} \\ I_3 &= 8\text{ A} \end{aligned}$$

results in the following solutions:

$$\begin{aligned} 2I_1 - 16I_2 + 8I_3 &= 0 \\ 2(6\text{ A}) - 16I_2 + 8(8\text{ A}) &= 0 \end{aligned}$$

and 
$$I_2 = \frac{76\text{ A}}{16} = \mathbf{4.75\text{ A}}$$

Then 
$$I_{2\Omega} \downarrow = I_1 - I_2 = 6\text{ A} - 4.75\text{ A} = \mathbf{1.25\text{ A}}$$


and 
$$I_{8\Omega} \uparrow = I_3 - I_2 = 8\text{ A} - 4.75\text{ A} = \mathbf{3.25\text{ A}}$$

Again, note that you must stick with your original definitions of the various mesh currents when applying Kirchhoff's voltage law around the resulting supermesh paths.



# Nodal Analysis


**EXAMPLE 8.23** Write the nodal equations for the network in Fig. 8.59.

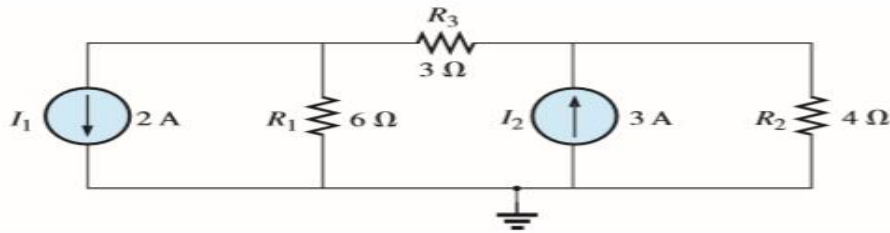

**FIG. 8.59**  
Example 8.23.

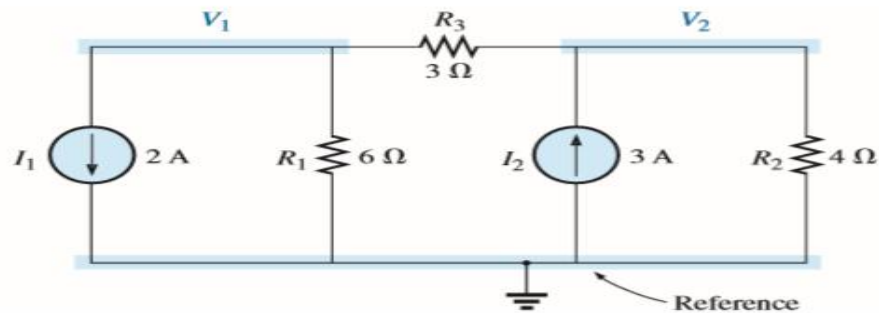**Solution:**

**Step 1:** Redraw the figure with assigned subscripted voltages in Fig. 8.60.



$$V_1: \underbrace{\left( \frac{1}{6\Omega} + \frac{1}{3\Omega} \right)}_{\text{Sum of conductances connected to node 1}} V_1 - \underbrace{\left( \frac{1}{3\Omega} \right)}_{\text{Mutual conductance}} V_2 = \overset{\substack{\text{Drawing current} \\ \text{from node 1}}}{\downarrow} -2\text{ A}$$


out going

$$V_2: \underbrace{\left( \frac{1}{4\Omega} + \frac{1}{3\Omega} \right)}_{\text{Sum of conductances connected to node 2}} V_2 - \underbrace{\left( \frac{1}{3\Omega} \right)}_{\text{Mutual conductance}} V_1 = \overset{\substack{\text{Supplying current} \\ \text{to node 2}}}{\downarrow} +3\text{ A}$$

in - coming



# Nodal Analysis

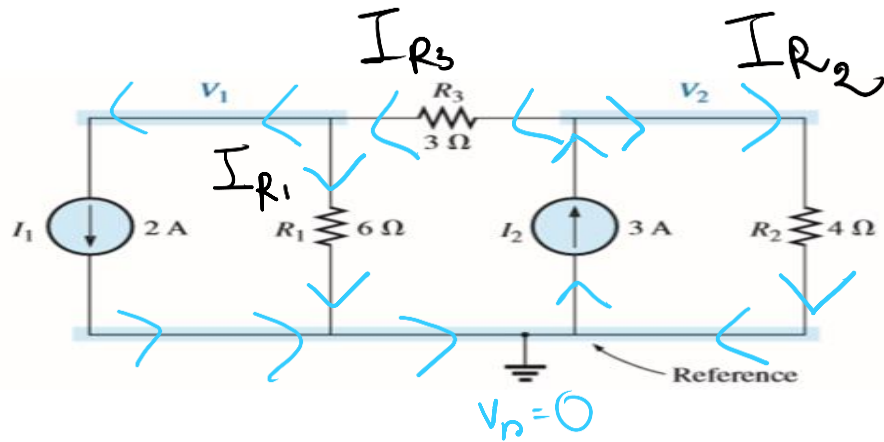

$$I_{R3} = I_1 + I_{R1}$$

$$\Rightarrow \frac{V_2 - V_1}{R_3} = 2 + \frac{V_1 - 0}{R_1}$$

$$\Rightarrow \frac{V_2 - V_1}{3} = 2 + \frac{V_1}{6}$$

$$I_{R3} + I_{R2} = I_2$$

$$\Rightarrow \frac{V_2 - V_1}{R_3} + \frac{V_2 - 0}{R_2} = 3$$

$$\Rightarrow \frac{V_2 - V_1}{3} + \frac{V_2}{4} = 3$$



Drawing current from node 1  
↓  
out going

$$V_1: \underbrace{\left( \frac{1}{6\Omega} + \frac{1}{3\Omega} \right)}_{\text{Sum of conductances connected to node 1}} V_1 - \underbrace{\left( \frac{1}{3\Omega} \right)}_{\text{Mutual conductance}} V_2 = -2\text{ A}$$

Supplying current to node 2  
↓  
in-coming

$$V_2: \underbrace{\left( \frac{1}{4\Omega} + \frac{1}{3\Omega} \right)}_{\text{Sum of conductances connected to node 2}} V_2 - \underbrace{\left( \frac{1}{3\Omega} \right)}_{\text{Mutual conductance}} V_1 = +3\text{ A}$$

# Another problem from Nodal Analysis

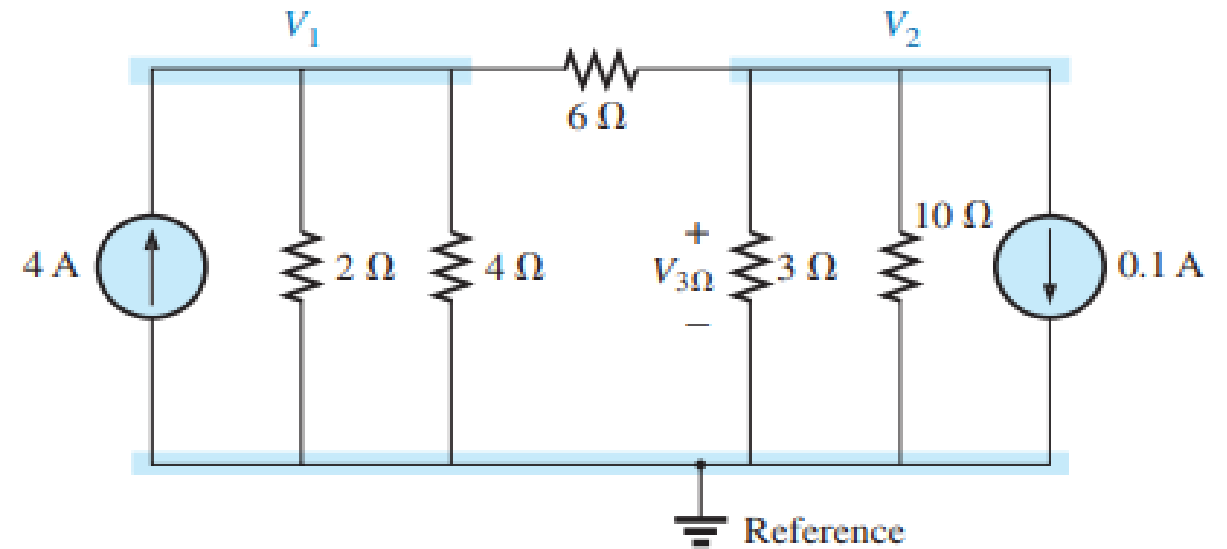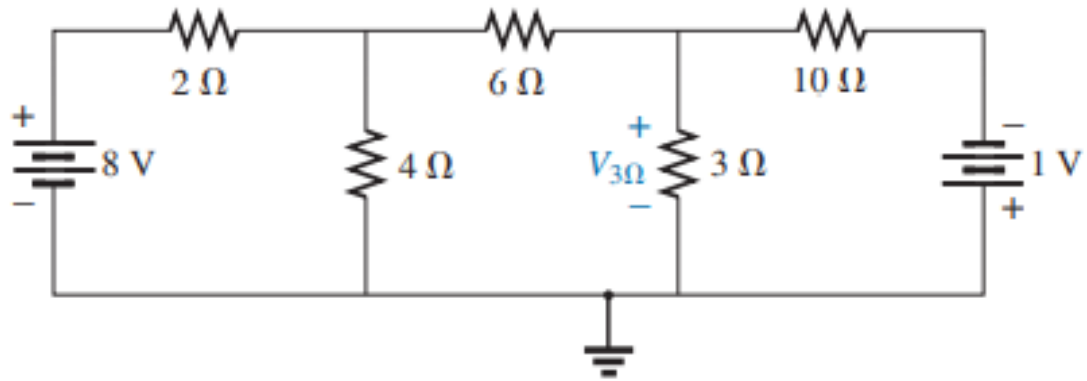


$$\left( \frac{1}{2\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{6\ \Omega} \right) V_1 - \left( \frac{1}{6\ \Omega} \right) V_2 = +4\ \text{A}$$

$$\left( \frac{1}{10\ \Omega} + \frac{1}{3\ \Omega} + \frac{1}{6\ \Omega} \right) V_2 - \left( \frac{1}{6\ \Omega} \right) V_1 = -0.1\ \text{A}$$

---

# Concept of Nodal Analysis

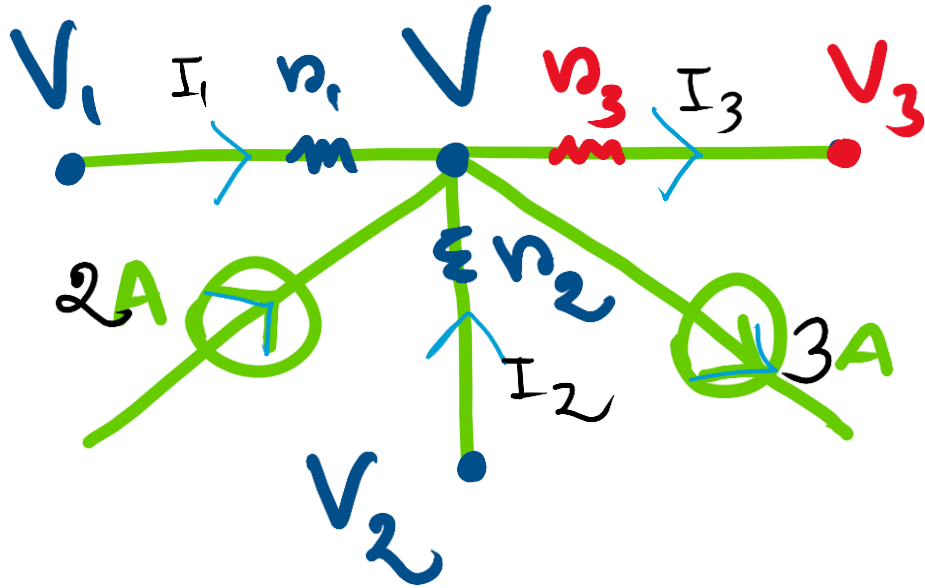


$$I_1 + I_2 + 2 = I_3 + 3$$

$$\Rightarrow \frac{V_1 - V}{R_1} + \frac{V_2 - V}{R_2} + 2 = \frac{V - V_3}{R_3} + 3$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} - V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + 2 - 3 = 0$$

$$\text{or, } V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) + 3 - 2 = 0$$

# Super Node

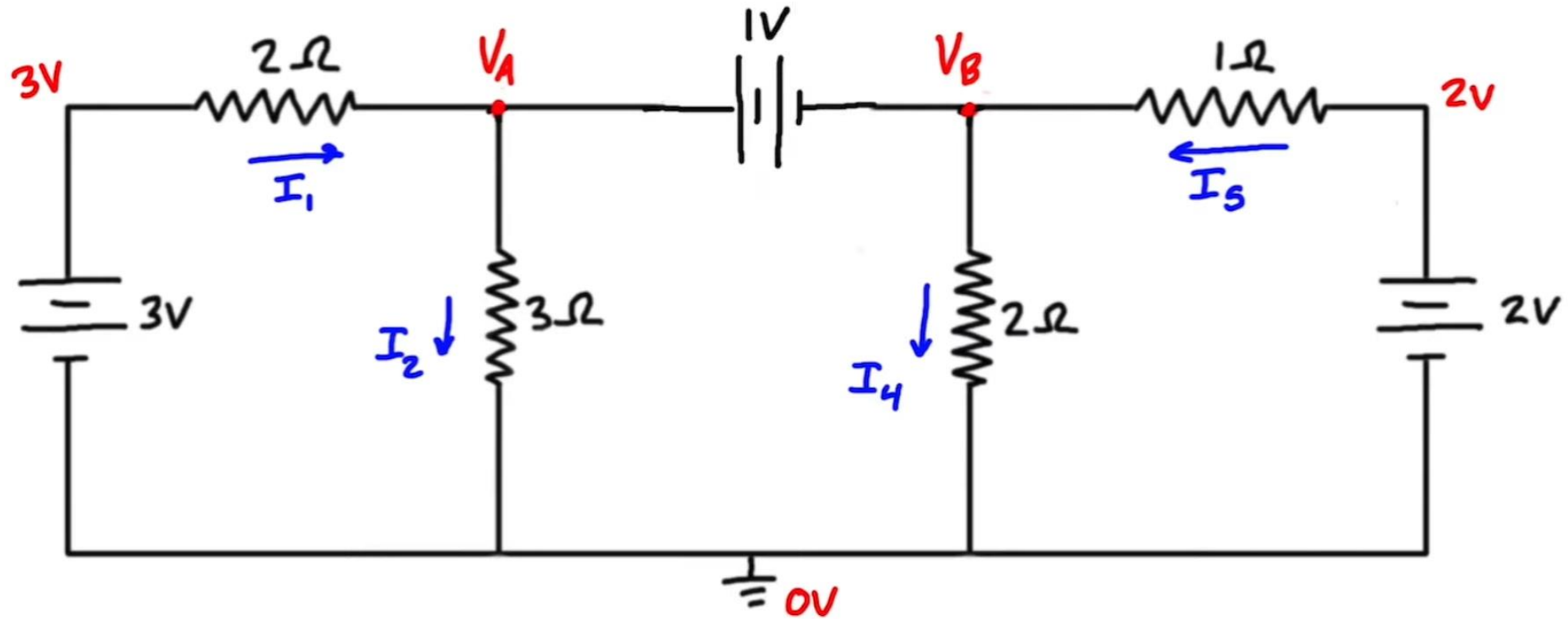


$$\text{KCL A: } I_1 = I_2 + I_3$$

$$\text{KCL B: } I_3 + I_5 = I_4$$

$$V = IR \quad I = \frac{V}{R}$$



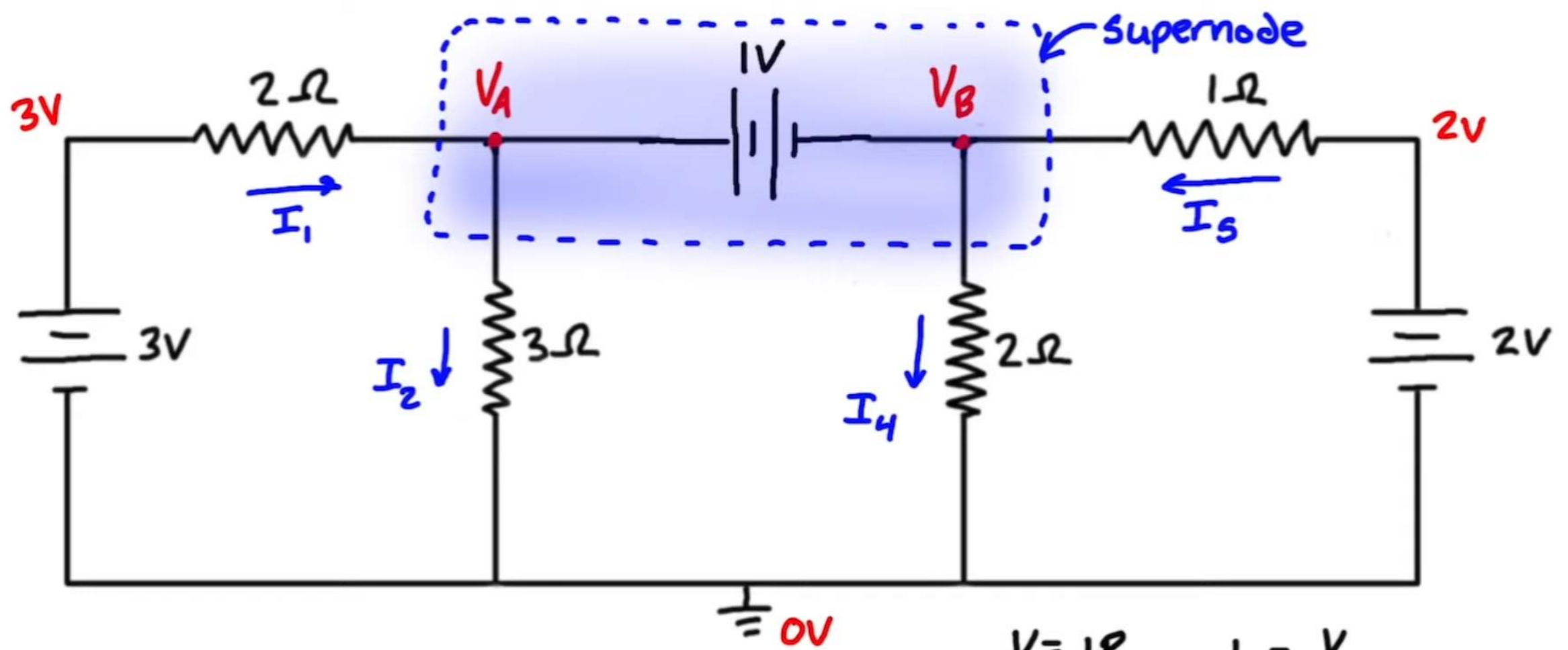

KCL supernode

$$I_1 + I_s = I_2 + I_4$$

$$\left( \frac{3V - V_A}{2\Omega} \right) + \left( \frac{2V - V_B}{1\Omega} \right) = \frac{V_A}{3\Omega} + \frac{V_B}{2\Omega}$$

$$V = 1R \quad I = \frac{V}{R}$$

Supernode equation

$$V_A = V_B + 1$$



**THANK YOU**